

## Errata

**Document Title:** Decreasing The Response Time of the Model 405 Input Filter  
(AN 41D)

**Part Number:** 5989-6246EN

**Revision Date:** December 1960

---

### HP References in this Application Note

This application note may contain references to HP or Hewlett-Packard. Please note that Hewlett-Packard's former test and measurement, semiconductor products and chemical analysis businesses are now part of Agilent Technologies. We have made no changes to this application note copy. The HP XXXX referred to in this document is now the Agilent XXXX. For example, model number HP8648A is now model number Agilent 8648A.

### About this Application Note

We've added this application note to the Agilent website in an effort to help you support your product. This manual provides the best information we could find. It may be incomplete or contain dated information, and the scan quality may not be ideal. If we find a better copy in the future, we will add it to the Agilent website.

### Support for Your Product

Agilent no longer sells or supports this product. You will find any other available product information on the Agilent website:

[www.agilent.com](http://www.agilent.com)

Search for the model number of this product, and the resulting product page will guide you to any available information. Our service centers may be able to perform calibration if no repair parts are needed, but no other support from Agilent is available.



# APPLICATION NOTES

## APPLICATION NOTE 41D

### DECREASING THE RESPONSE TIME OF THE MODEL 405 INPUT FILTER

The input filter of the Model 405 is designed primarily for maximum ac rejection compatible with reasonable response time to a step function. The ac rejection at 60 cps is typically about 50 db while the response time to a step of voltage is less than a second - normally 750 milliseconds.

The response time of the filter can be reduced to make it compatible with the maximum sampling rate where there are only 200 milliseconds between successive samplings. CAUTION: with filter response times this low the ac rejection at 60cps will typically be only 10 db. Extra care must be taken to be sure

that high level 60 cps signals are not present on the voltage being measured low.

Modification 1 - To reduce the response time on the  $\pm .999$  volt range, remove C1 and replace C2 with a  $0.01 \mu\text{f}$ , 1000 vdcw polystyrene capacitor. For convenience, two  $0.02 \mu\text{f}$  600 vdcw capacitors may be used in series.

Modification 2 - To reduce the response time on all ranges, perform Modification 1 and in addition remove C3 and replace with a  $0.01 \mu\text{f}$ , 600 vdcw polystyrene or mylar dielectric capacitor.

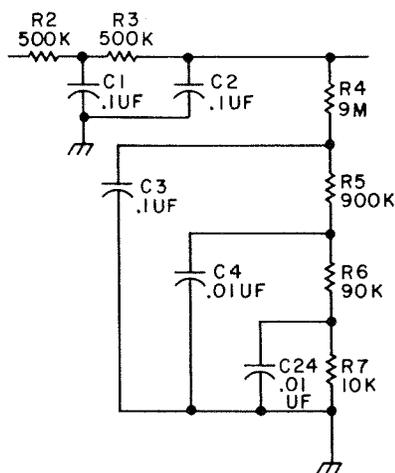


Figure 1.

Input Filter as Furnished on 405

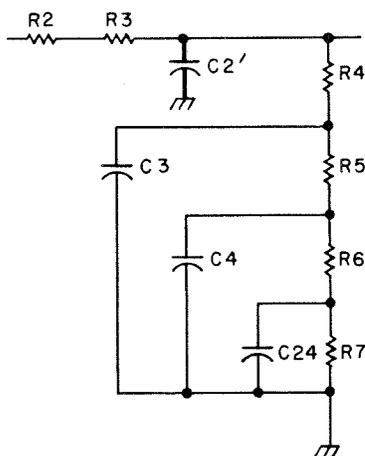


Figure 2.

Input Filter Modified for Fast Response on  $\pm .999$  V Ranges

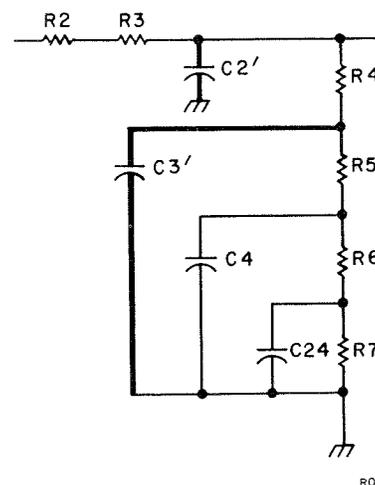


Figure 3.

Input Filter Modified for Fast Response on all Ranges

12/1/60